

ATG FOR SSFs IN SEQ. CIRCUITS

TEST OF BRIDGING FAULTS

Weidong Li

*Electronics System, Dept. of EE.
Linköping University, Sweden*

Testing of Digital Systems, 2000-11-29


ATG FOR SSFs IN SEQUENTIAL CIRCUITS

- ✗ Introduction
- ✗ TG using iterative array models
- ✗ Simulation-based TG
- ✗ Random TG
- ✗ Other TG methods

● Introduction

✗ Sequential circuits:

 Synchronous seq. circuits and **asynchronous** seq. circuits



✗ What make(s) differences?

States: controllability (how to ensure state q) and observability (how to know state $q+$)

State for sure?

● TG Using Iterative Array Models

✗ Basic instinct

State \Rightarrow Stateless

✗ Terminology

Iterative combinational array: Unrolling of syn. seq. circuits into combinational cell array.

* time domain \Rightarrow space domain

Time frame: each cell in iterative comb. array (both state and PIs at certain clk period).

✗ TG using iterative array models

Direct extension of from combinational circuits:

* Target Fault \Rightarrow Combinational test vector & Error propagation

* Combinational vector \Rightarrow PIs and State q (line justification)

* “Justify” state q (state initiation)

* Error propagation \Rightarrow POs and State q+

* POs \Rightarrow Bingo! State q+ \Rightarrow “propagate” q+ to POs

Known initial state \Rightarrow state generation from initial state \Rightarrow NP-problem

Unknown initial state \Rightarrow state learning (self-initialization) \Rightarrow NP-problem

● TG Using Iterative Array Models (cont.)

✗ General algorithm (Under assumption that clock line is fault-free)

```

r=1
repeat
  Begin
    Build model with r time frames
    ignore the POs in the first r-1 frames
    ignore the q+ outputs in the last frame
    q(1)=given initial state
    if (test generation success) then return
      SUCCESS
    r=r+1
  end
until r=fmax
return FAILURE

```

Algorithm for known initial state

f_{max}: maximum number of frames, determined by cost function.

```


r=1
p=0
repeat
  begin
    build model with p+r time frames
    ignore the POs in the first p+r-1 frames
    ignore the q+ outputs in the last frame
    if (test generation success) and every q
      input in the first frame has value x)
      then return SUCCESS
    increment r or p
  end
until (r+p=fmax)
return FAILURE

```

Algorithm for unknown initial state

● TG Using Iterative Array Models (cont.)

✕ Example 6.18:

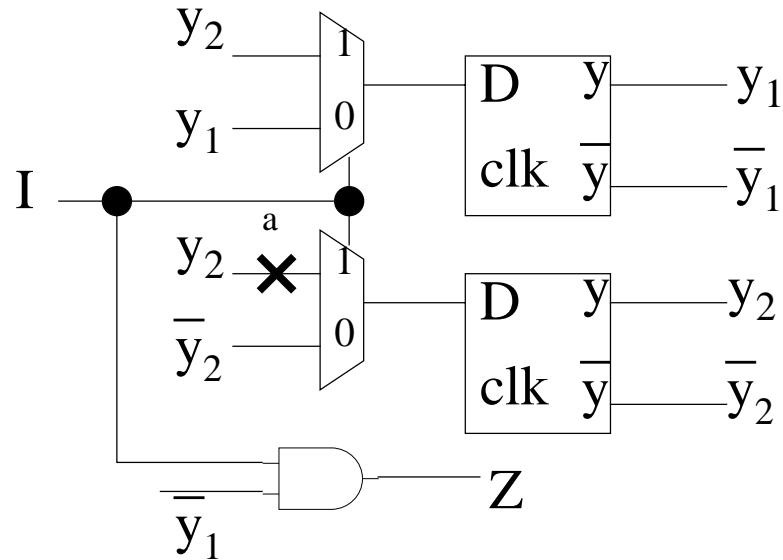

line a: s-a-1 fault. Known state (0, 0).

Time frame 1:

Fault activation: $I(1)=1$.


Fault propagation \Rightarrow PO Z: $y2 \Rightarrow y1 \Rightarrow Z$

Time frame 2:

$I(2)=1$: $y2(1) \bar{D} \Rightarrow y1(2)$.

Time frame 3:

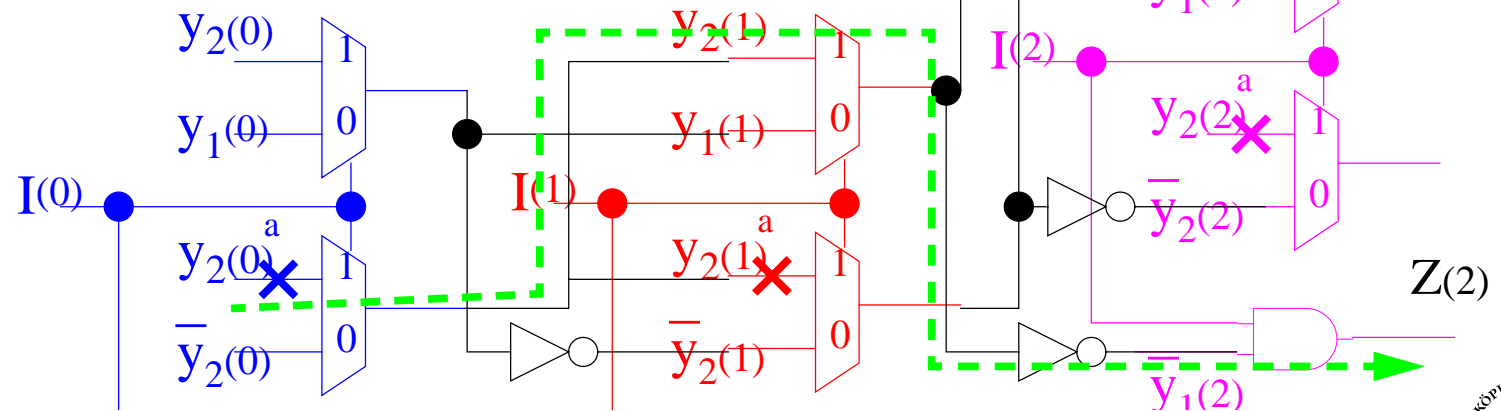$I(3)=1$: $\bar{y}1(2)$: $D \Rightarrow Z$



● TG Using Iterative Array Models (cont.)

✗ Drawbacks:

- * non a priori problem (unknown r/p)
- * Discard of $r-1$ ($r+p-1$) computations \Rightarrow reuse
- * Fault absorption could cause infinite loop \Rightarrow state monitor and/or f_{\max} .

● TG Using Iterative Array Models (cont.)

✗ EBT (Extended BackTrace)

- * Don't like $r > 0$

- * Increase only p

✗ Critical-path TG

- * Start with a known state (reset)

- * Start with fault activation, search the error propagation path towards POs

● TG Using Iterative Array Models (cont.)

✗ Clock(s)

Fault at clock line => No state updating

Explicit clock line

Propagate both $1/q_i$ and $0/q_i$ fault effect to POs (?)

✗ Complexity issues

Relative to

- * number of cycles
- * number of F/Fs per cycle
- * number of cycles a F/F is involved in

MUCH MORE COMPLICATED

● Asynchronous circuits

✗ Difficulties

Race problem

Why it is less in synchronous circuits?

Feedback identification

Delay variation

✗ Iterative models

PIs do not change until stable state is reached.

✗ Discussion

“Global asynchronous, local synchronous” is a favour strategy for SoC. As observed from above, the asynchronous circuits are much difficult for testing. How to meet this challenge?

● Simulation-Based TG

✕ Principle

- ◆ Generate test vectors
Random generate or non random generate
- ◆ Evaluate cost of test vectors according to the simulation
- ◆ Select test vectors to test sequence

✕ Cost function evaluation [Agrawal88]

- ◆ Initialization: number of F/Fs with unknown state.
- ◆ TG for group faults: summarize all cost value of activated faults.
- ◆ TG for individual faults: measurement from current state.

Heuristic optimization

● TG Using RTL Models

Know functionality of component, don't care or unknown gate-level model.

✗ Extensions of *D*-Algorithm

- ◆ Keep overall structure, extend operations.
 - ◆ Line-justification: find **operation** set to create fault.
 - ◆ Implication based on component **operators** at RTL (state).
 - ◆ Error-propagation: find **operation** set that propagate fault to output registers.
In text book, the output registers are limited to data output (?).
- Advantage:
 - ◆ Higher level ==> increase the efficiency
 - ◆ IP-core
 - ◆ Suitable for DFT methods like scan-test etc.
 - Disadvantage:
 - ◆ Limited to operations

● TG Using RTL Models (cont.)

✕ Heuristic State-Space Search

SCIRTSS(Sequential CIRcuit Test Search System)

- ◆ Separation of datapath and control-part
- ◆ Utilize combinational TG to activate fault
- ◆ Find state set to propagate the fault involving heuristic function

$$H_n = G_n + wF_n$$

G_n : sequence length, w : weight, F_n : heuristic function.

F_n : fault proliferation function, or distance to goal node, or state trans.

● Random TG

✗ Problem

- ◆ Initialization: initial state requires a deterministic sequences
- ◆ “Coloured lines: control lines are more weighted
- ◆ Evaluation

✗ Solution

- ◆ Initialization difficulty ==> semirandom
- ◆ “Coloured lines”==> nonuniform signal probability
- ◆ Evaluation ==> modify the goal function, take account of propagation

● Other TG Methods

✕ Hardware support for TG

- ◆ Advantage: concurrence
- ◆ Disadvantage: reuse?

✕ Artificial intelligence techniques

- ◆ HITEST: combines algorithmic procedures and user-provided knowledge

TESTING OF BRIDGING FAULTS



- ✗ Bridging-fault model
- ✗ Detection of NFBFs
- ✗ Detection of FBFs
- ✗ BFs simulation
- ✗ TG for BFs

● Bridging-Fault Model

✗ Bridging fault

Faults are caused by **shorts** between two (or more) normally unconnected signal lines.

✗ Bridging-fault model

  

Logic function $Z(x, y)$

✗ BF model used in text book

- ◆ $Z(x, y) = x.y$ AND BFs
- ◆ $Z(x, y) = x+y$ OR BFs

✗ Multiple bridging-fault model

Multiple signal lines **short**

- ◆ AND/OR BFs?

Enough with this model? (Resistive BF model, Pattern dependent model etc.)

✗ Fault activation

Short signal lines must have different logic values.

Behave differently from proposed function.

● Detection of NFBFs

✕ AND NFBFs

- ◆ Non Feedback Bridging Faults: No combinational loop.
- ◆ Theorem 7.1: bridge between SSFs and BFs.
A test detects the (x,y) iff either t detects x s-a-0 and sets $y=0$ or sets $x=0$ and y s-a-0.
- ◆ Corollary 7.1: Fanout-free x and y are inputs to the same OR/NOR gate, then the AND BF(x,y) dominates both x s-a-0 and y s-a-0.
- ◆ Corollary 7.2: Let x be a line with fanout and y a line without. If x and y are inputs to the same OR/NOR gate, then the AND BF(x,y) dominates y s-a-0.

● Detection of FBFs

✗ AND FBFs

- ◆ Combinational logic \implies sequential logic
(Loop \implies Oscillation possible)
- ◆ Theorem 7.2: A test t detects f s-a-0 and sets $b=0$ detects the AND FBF($b.f$).
- ◆ Theorem 7.3: A test t detects b s-a-0 and sets $f=0$ without sensitizing f detects the AND FBF($b.f$).
- ◆ Corollary 7.3: Let $(b.f)$ be an AND FBF such that **all** paths between b and f have even inversion parity. A test t detects either f s-a-0 and sets $b=0$, or b s-a-0 and sets $f=0$, also detects $(b.f)$.
- ◆ Corollary 7.4: Let $(b.f)$ be an AND FBF such that **any** path between b and a primary output goes through f . A test t detects $(b.f)$ iff t detects f s-a-0 and sets $b=0$.

● Detection of FBFs(cont.)

✕ AND FBFs(cont.)

- ◆ Corollary 7.5: Let $(b.f)$ be an AND FBF where b and f are such that $f=1$ whenever $b=0$ (in the fault-free circuit). A test t detects $(b.f)$ iff t detects f s-a-0 and sets $b=0$.
- ◆ Corollary 7.6: No signal test can detect an AND FBF $(b.f)$ such that every path between b and a primary output goes through f , and $f=0$ whenever $b=0$.

● Bridging Faults Simulation

✗ Complexity (compare with SSFs)

- ◆ Structure and function
- ◆ The number of feasible BFs

✗ Implicit simulation method

- ◆ Based on relation between BFs and SSFs
- ◆ Layout information available ==> Complexity reduction!
- ◆ AND BFs: detects x s-a-0, find possible sets y $y=0$ in the neighbours, check propagation path.

Good fault coverage of SSFs ==> good fault coverage of BFs?

● TG for BFs

✕ TG of BFs = SSFs + sets

- ◆ Based of relationship of BFs and SSFs
- ◆ Generate TG for x s-a-v
- ◆ Justify $y = \bar{v}$
- ◆ FBFs: find $y = \bar{v}$ between x 's successors and implications

Of the same complexity order.