

Built-In Self-Test (BIST)

Abdil Rashid Mohamed, abdmo@ida.liu.se
Embedded Systems Laboratory (ESLAB)
Linköping University, Sweden



Introduction

- BIST --> Built-In Self Test
- BIST - part of the circuit (chip, board or system) is used to test the circuit itself
 - *V. Agrawal defines BIST as a DFT technique in which testing (test generation and test application) is accomplished through built-in hardware features*
- BIST = BIT (Built in test) + self test



Advantages of BIST

- *fast, efficient and hierarchical* - same hardware is capable of testing chips, boards and systems.
 - At system level BIST is a cheap test solution
 - alternative test solutions are *chip-wise and system-foolish*
- No need of expensive ATE (cost \geq \$10 million)
- testing during operation and maintenance
- uniform technique for production, system and maintenance tests
- dynamic properties of the circuit can be tested at speed
- support concurrent testing
- can be used for *delay testing* as it can be used in real time




Problems with BIST


- Additional BIST hardware overhead
- Performance degradation, timing problems
- additional delay and elongated critical path



Basic BIST Principle

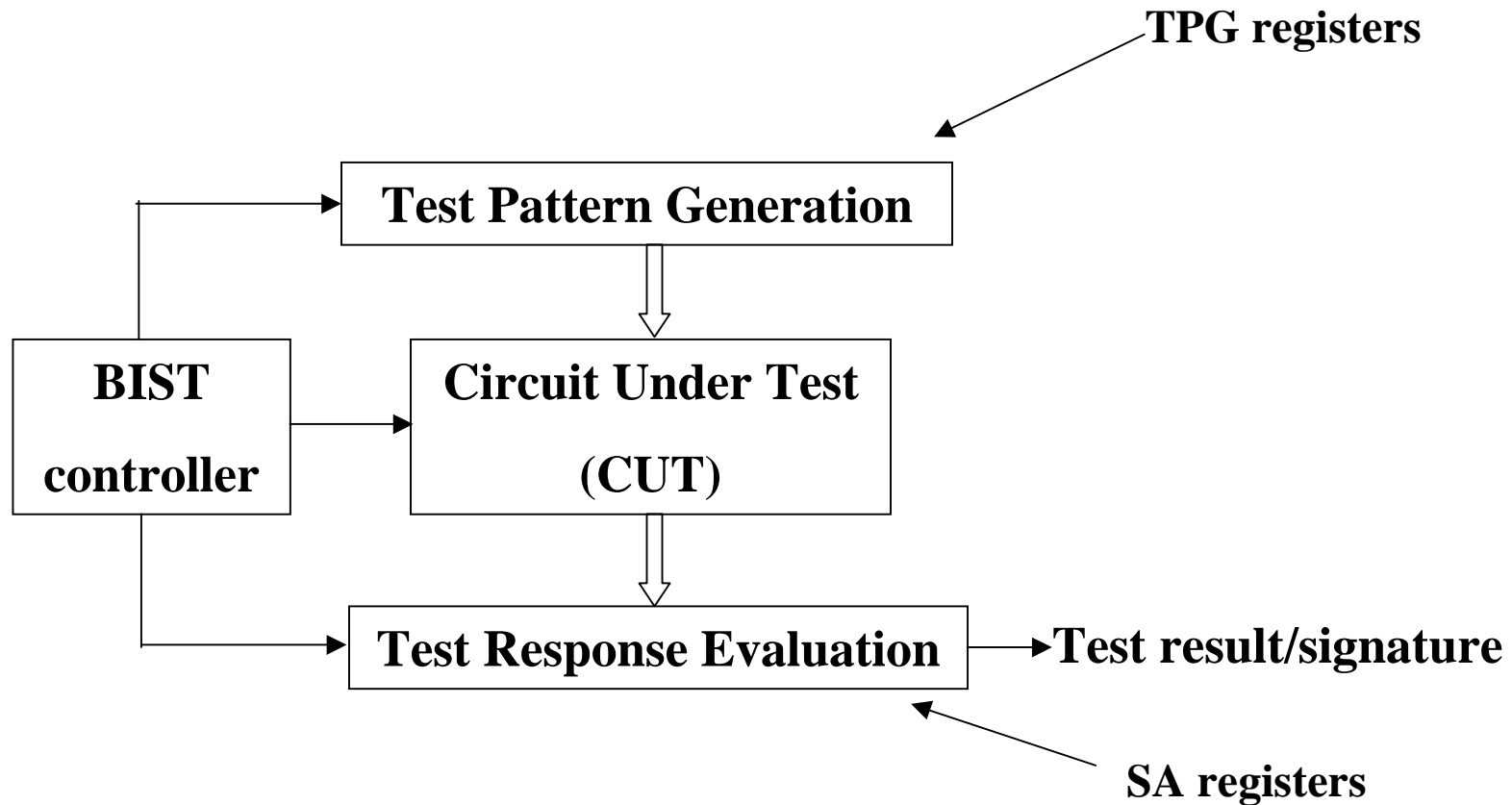

BIST Classification

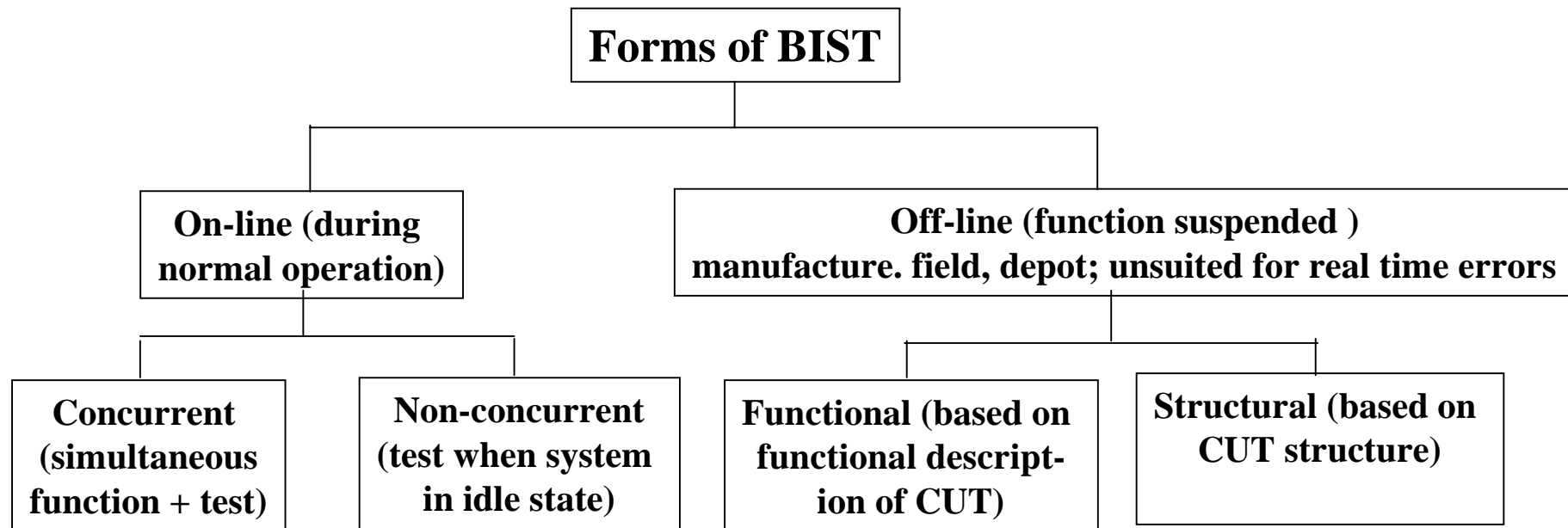

Glossary of BIST Test Structures

- TPG – test pattern generator □ generates test vectors on-chip
 - PRPG – pseudorandom PG □ generates random, but biased vectors
 - LFSR – Linear feedback shift register □ commonly used PRPG
 - SRSG – shift register sequence generator □ single output PRPG
- ORA – (generic) output response analyzer
 - SISR – single input signature register
 - MISR – multiple input signature register
- BILBO – Built in Logic Block Observer □ non-simultaneous PG & SA
- CBILBO – Concurrent BILBO □ simultaneous PG & SA
 - too big !



BIST Hardcore

- *Hardcore* -
 - Part of the circuit that must be operational to perform self test
 - Power supply, ground, clock circuitry, etc.
- Self test failure
 - CUT fails, or
 - Hardcore is faulty
- Hardcore is tested by:
 - external ATE or
 - made self testable by *redundancy* such as *duplication* or *self checking logic*



Levels of Self Test

- Production testing of newly manufactured components
 - Levels: chip □ board □ system
 - with *boundary scan* BIST can be used at all levels of system
- Field testing
 - BIST can diagnose faults down to field-replaceable units – no ATE
 - Improves **maintainability and life cycle cost** of hardware
 - **2-level maintenance** -
 - system performs a self test, and
 - automatic diagnosis of faults to field replaceable units, such as boards.



Test Pattern Generation for BIST

- 1. Exhaustive testing
 - exhaustive test-pattern generators
- 2. Pseudorandom testing
 - weighted and adaptive test generator
- 3. Pseudoexhaustive testing
 - Counters: syndrome driver & constant weight
 - combined LFSR and shift register
 - combined LFSR and XOR gates
 - Others: condensed LFSR, cyclic LFSR, etc.



1. Exhaustive Testing

- Assume CUT: *n-input, m-output combinational*
- Applies all 2^n input test vectors
 - complete testing for all static faults
 - detects all detectable faults
- Suitable TPGs
 - binary counters
 - max. length autonomous LFSR (*complete LFSR*) modified to include an all-0s state
- Drawbacks:
 - unfeasible if $n > 22$ □ too many test vectors
 - not applicable to sequential circuits




2. Pseudorandom Testing

- Test patterns: $< 2^n$
 - random, but deterministic and repeatable
 - autonomous LFSR is used
- Generation
 - with replacement(pattern generated more than once) or
 - without replacement (each pattern is unique)
- FC can be determined by *fault simulation*
- An acceptable level of FC is obtained by selecting suitable Test length
- Random resistant faults
 - long test lengths to insure high FC
- LFSR produces test patterns with equal no. of 0's and 1's on each input line
- Biased distribution of 0's and 1's captures more faults, \uparrow FC, \downarrow test vectors



Weighted Test Generation

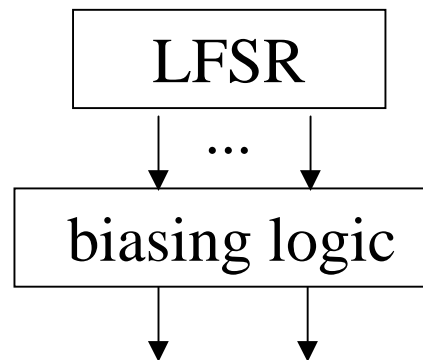- TPG with *non-uniform* distribution of 0's and 1's on the output lines
 - change prob. Of a 0 or 1 to improve FC
 - For example: LFSR \square Prob(0) = Prob(1) = 0.5
 - Weighted LFSR \square Prob(0) = 0.25; Prob(1) = 1- Prob(0)
- Pre-process procedure is used to determine the weights and design weighting circuitry
- Constructed using an autonomous LFSR and combinational circuit



Adaptive Test Generation

- Employs a weighted TPG
- Use fault simulation results to modify the weights
 - one or more probability distributions for the test patterns
- a TPG is designed based on the probability distributions above
- Adaptive TPG
 - efficient in terms of test length, but
 - hardware can be complex




3. Pseudoexhaustive Testing

- All benefits of exhaustive testing, but *fewer test patterns*
- Idea: Segment *circuit* and *exhaustively test* each segment
 - logical segmentation
 - cone segmentation (verification testing)
 - sensitized path segmentation
 - physical segmentation
- To test n-input circuit
 - reconfigure input lines to generate tests on m lines ($m < n$)
 - M lines –*test signals*- fan out and drive the n lines to CUT




Cone segmentation

- Cone segmentation (verification testing)
 - Segment m output circuit into m cones,
 - cone consist of logic associated with *one output*
 - test each cone exhaustively
 - all cones are tested concurrently
- An example of an (n,w) -CUT = $(4,2)$ -CUT
 - $y_1=f_1(x_1,x_3)$; $y_2=f_2(x_1,x_2)$; $y_3=f_3(x_2,x_3)$; $y_4=f_4(x_3,x_4)$
 - 4 cones y_1, y_2, y_3 & y_4 tested concurrently
 - 4 test vectors to each cone

 

Sensitized-path segmentation

 


- Segmentation based on *path sensitization*
- Exhaustive test of C1 –
 - establish sensitized path from C to F by:
 - Apply 2^{n_1} patterns to A
 - Set B such that $D = 1$
 - AND gate is also tested
- Similar testing for C2
- Effective testing using only $2^{n_1} + 2^{n_2} + 1$ test vectors instead of $2^{n_1+n_2}$
- If A, B \rightarrow PRPG, F \rightarrow MISR,
 - BIST hardware sharing is achieved



Identification of Test Signal Inputs

- *P-test signals* drive all N -inputs of circuit, $p < n$.
- Some of p lines fan-out to one/more of the normal input lines
- Exhaustive test of multiple output function (f, g) needs 8 test vectors
- 4 test vectors test the two functions, f and g , exhaustively and concurrently
 - No output is a function of both x and z
 - Same test data can be applied to both lines x & z \square one test signal
 - Circuit testable using only two test signals
 - Verification test inputs $x=z$


 


Procedure - Identify Minimal Set of Test Signals

- **Step 1:** Partition the circuit into disjoint subcircuits
- **Step 2:** For each disjoint subcircuit
 - Generate a dependency matrix, D
 - Partition D into groups of inputs so that two/more inputs in a group do not affect same output
 - Collapse each group to form an equivalent input, called a test signal input.
- For n-input, m-output circuit, dependency matrix $D = [d_{ij}]$; m rows, n columns
 - $D_{ij} = 1$ if output i depends on input j; otherwise $d_{ij} = 0$
- **Step 3:** Extract from Dc: number of partitions (width, p) and maximum number of 1s in the row (weight, w).
 - P represents max. no. Of input signals to test a disjoint subcircuit
 - W represents max. no. Of signals on which any output depends
 - Thus, pseudoexhaustive test length, L is given by: $2^w \leq L \leq 2^p$
- **Step 4: construct test patterns**



Example

  

$$D = \begin{array}{ccccccc|c} & a & b & c & d & e & f & g & \\ \hline & 1 & 1 & 0 & 0 & 1 & 0 & 0 & f_1 \\ & 0 & 1 & 1 & 0 & 0 & 0 & 1 & f_2 \\ & 1 & 0 & 0 & 1 & 1 & 0 & 0 & f_3 \\ & 0 & 0 & 1 & 1 & 1 & 0 & 0 & f_4 \\ & 0 & 0 & 0 & 0 & 1 & 1 & 0 & f_5 \end{array}$$

$$D_{gc} = \begin{array}{cc|cc|cc|c} & \text{I} & & \text{II} & & \text{III} & & \text{IV} & \\ \hline & a & c & b & d & e & f & g & \\ \hline & 1 & 0 & 1 & 0 & 1 & 0 & 0 & f_1 \\ & 0 & 1 & 1 & 0 & 0 & 0 & 1 & f_2 \\ & 1 & 0 & 0 & 1 & 1 & 0 & 0 & f_3 \\ & 0 & 1 & 0 & 1 & 1 & 0 & 0 & f_4 \\ & 0 & 0 & 0 & 0 & 1 & 1 & 0 & f_5 \end{array}$$

- Less than two 1s in each row and no. Of groups should be minimal
 - No output is driven by more than one input from each group
- Collapsed equivalent matrix, D_c , OR-ing each row in a group to form a single column



$$\Rightarrow D_c = \begin{array}{cccc|c} & \text{I} & \text{II} & \text{III} & \text{IV} & \\ \hline & t_1 & t_2 & t_3 & t_4 & \\ \hline 1 & 1 & 1 & 0 & f_1 \\ 1 & 1 & 0 & 1 & f_2 \\ 1 & 1 & 1 & 0 & f_3 \\ 1 & 1 & 1 & 0 & f_4 \\ 0 & 0 & 1 & 1 & f_5 \end{array}$$

- Number of partitions in Dc (width), $p=4$
 - p - max. no. of input signals to test disjoint subcircuit
- max. no. of 1's in any row (weight), $w=3$
 - max. np. Of signals on which any output depends
- Thus, pseudoexhaustive test length, L is given by: $2^w \leq L \leq 2^p$



Coffee Break



TPG for Pseudoexhaustive Tests

- Counters
 - Syndrome drive counter
 - constant weight counter
- Linear Feedback Shift Registers (LFSRs)
 - combined LFSR/SR
 - combined LFSR/XOR gates




Constant Weight Counter


- Constant weight counter
 - *N-out-of-M* code
 - A set of codewords of M-bits, where each codeword has N 1s.
- E.g. 2-out-of-4 CWC is: *1100, 1010, 1001, 0110, 0101, 0011*
- Any (n,w) circuit can be pseudoexhaustively tested by a constant-weight counter implementing a *w-out-of-K* code, for an appropriate value of K.
- For large values of N and M,
 - constant weight counter is too complex high.



Combined LFSR/SR

 


An LFSR/SR verification test generator

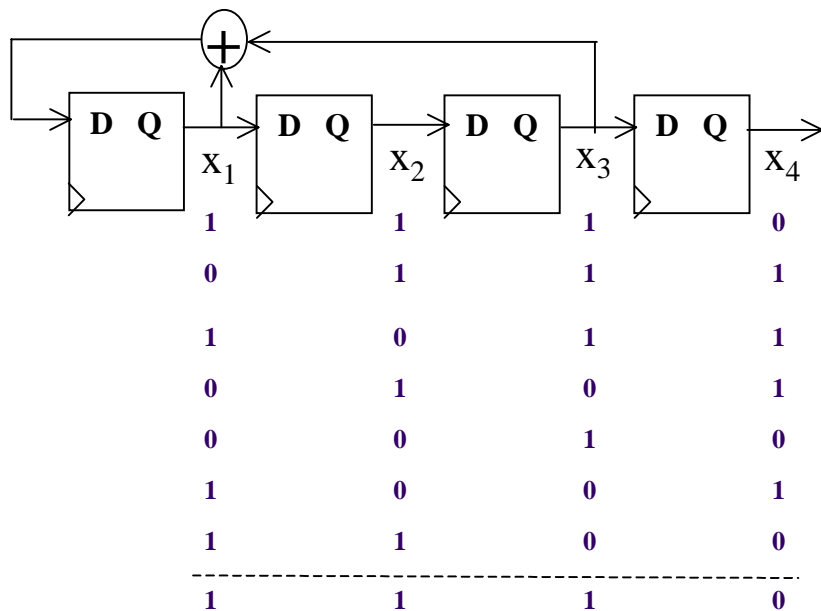

- Combination of LFSR and SR
- Advantages and drawbacks
 - cheaper than a constant weight counter,
 - number of vectors is near minimal when $w \ll n$, e.g $w < n/2$
 - generates more test vectors and LFSR needs at least 2 seed values
- On the left - 4-stage combined LFSR/SR for testing a (4,2)-CUT




Combined LFSR/XOR Gates

 

An LFSR/XOR verification test generator

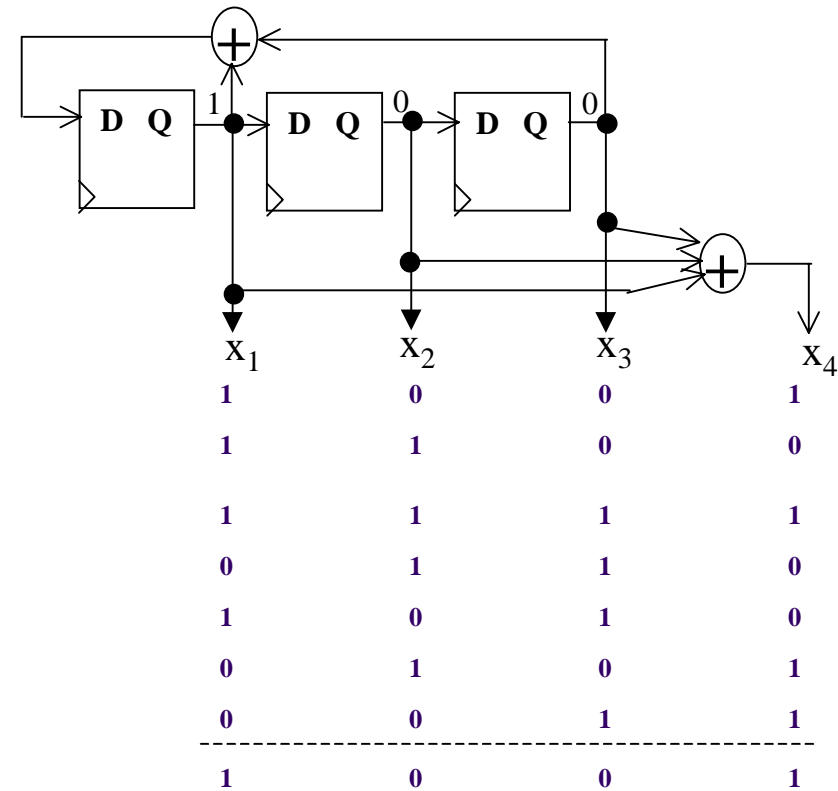- combination of LFSR and XOR gates (linear) network
 - based on *linear sums or linear codes*
 - Requires at most two seeds
 - no. of patterns approaches that required for LFSR/SR
- example design for testing a (4,2) CUT




Physical Segmentation


- Pseudoexhaustive methods □ large test sets for large circuits
- Employ physical segmentation to achieve pseudoexhaustive test sets
- Circuit is partitioned using hardware segmentation techniques
 - Chapter 9 □ partitioning circuit to reduce test generation cost
 - Insert **bypass storage** cells in some signal lines
 - bypass storage cell acts as a wire in normal mode and as part of LFSR in test mode
- **Bypass cell on line x** □
 - If associated LFSR is PRPG it generate test patterns on x
 - If associated LFSR is MISR it detect errors on x





Adding bypass storage cells

 


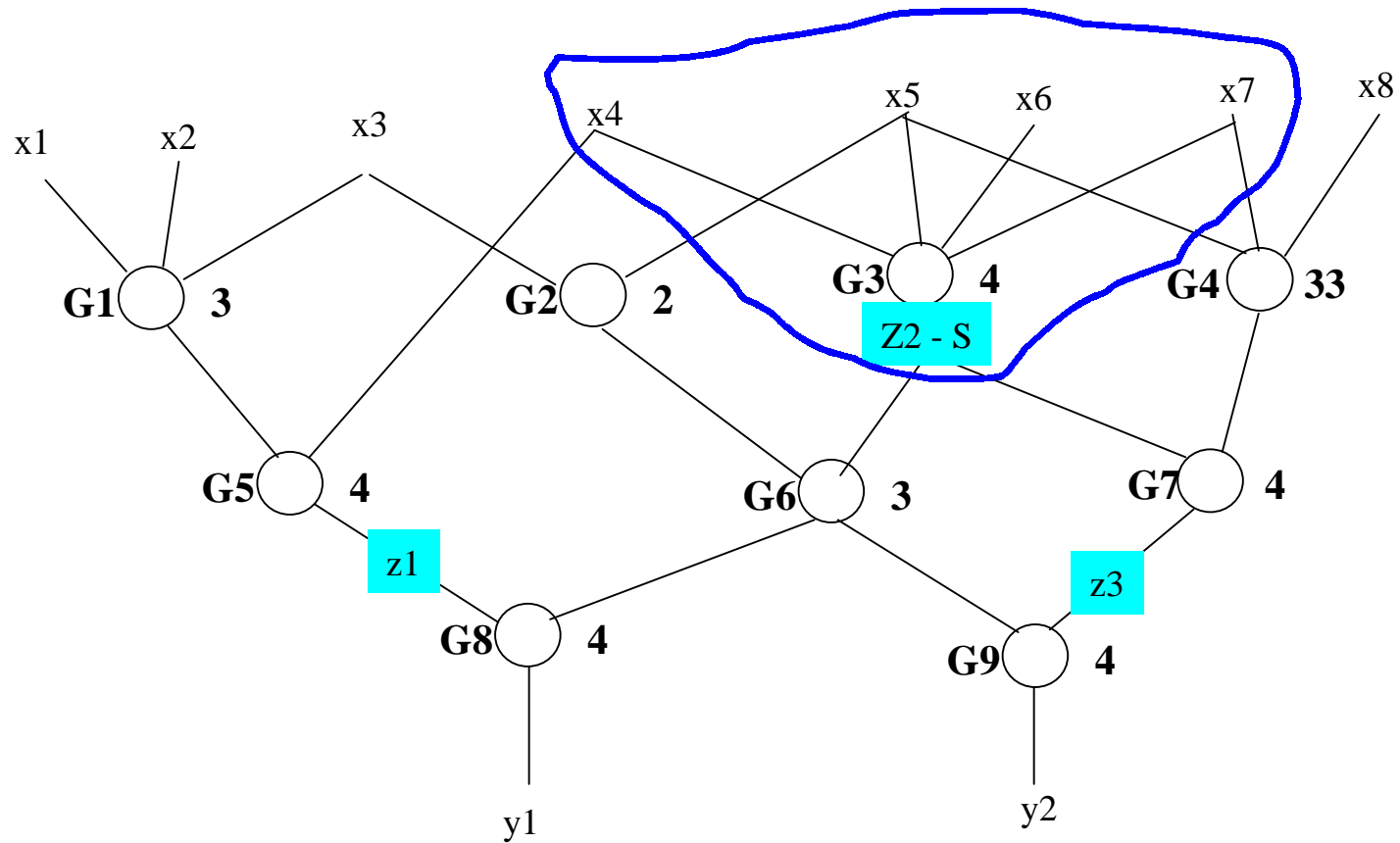- Segment circuit such that each signal is a function of not more than 4 variables



 

 

 


Generic-Off Line BIST Architectures

- BIST architecture
 - BIST structures for testing chips and boards consisting of blocks of combinational logic interconnected by storage cells
- BIST architecture components
 - TPGs, ORAs, CUT
 - Distribution system (DIST) for data: TPGs to CUT and CUT to ORAs
 - Interconnections(wires), busses, multiplexers and scan paths
 - BIST controller for controlling the BIST circuitry and CUT during BIST mode
- Type 1: **Centralized or distributed BIST** architecture
- Type 2: **Embedded or separate BIST** architecture




Centralized and Separate BIST architecture

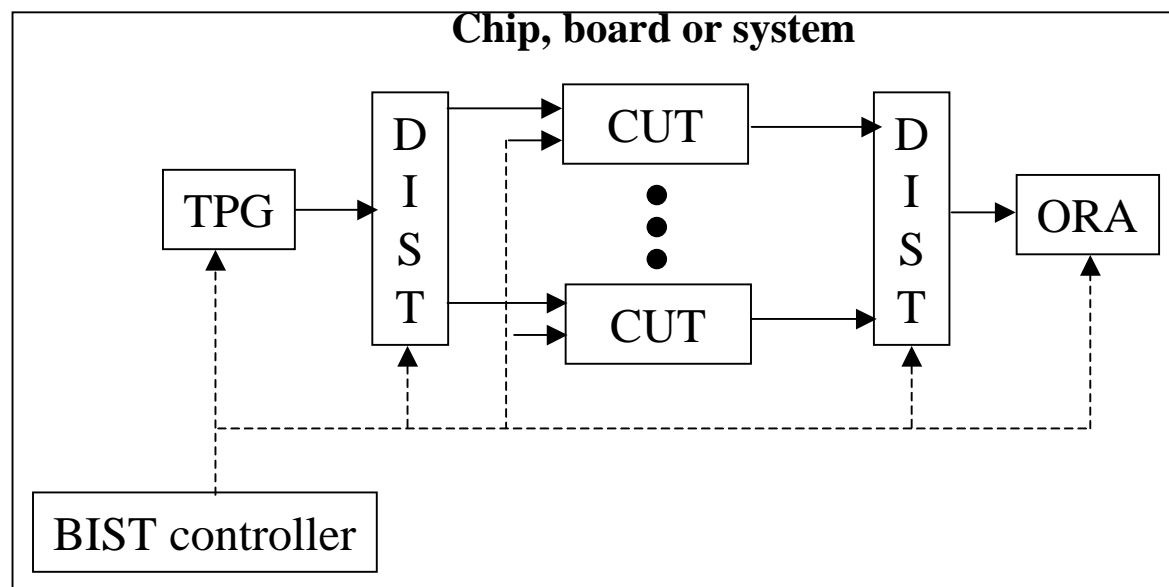- Several CUTs share TPGs and ORAs
 - Reduced overhead
 - Increased testing time
 - separate architecture - BIST circuitry is external to CUT and not part of functional circuitry




Distributed and Separate BIST architecture

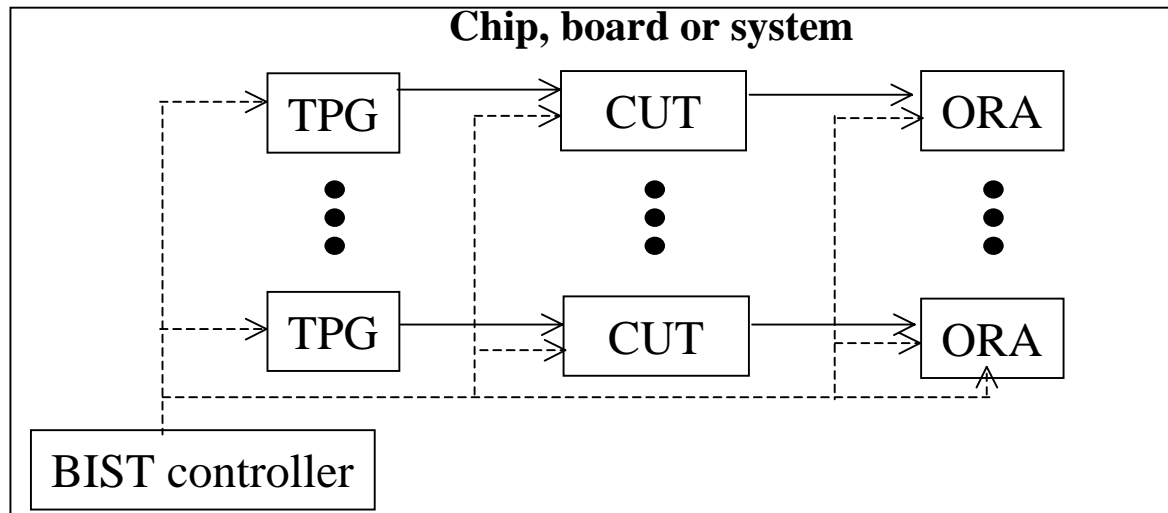- Each CUT has its own TPGs and ORAs circuitry
 - more overhead
 - reduced test time and accurate diagnosis
 - separate architecture - BIST circuitry is external to CUT and not part of functional circuitry



Distributed and Embedded BIST Architecture

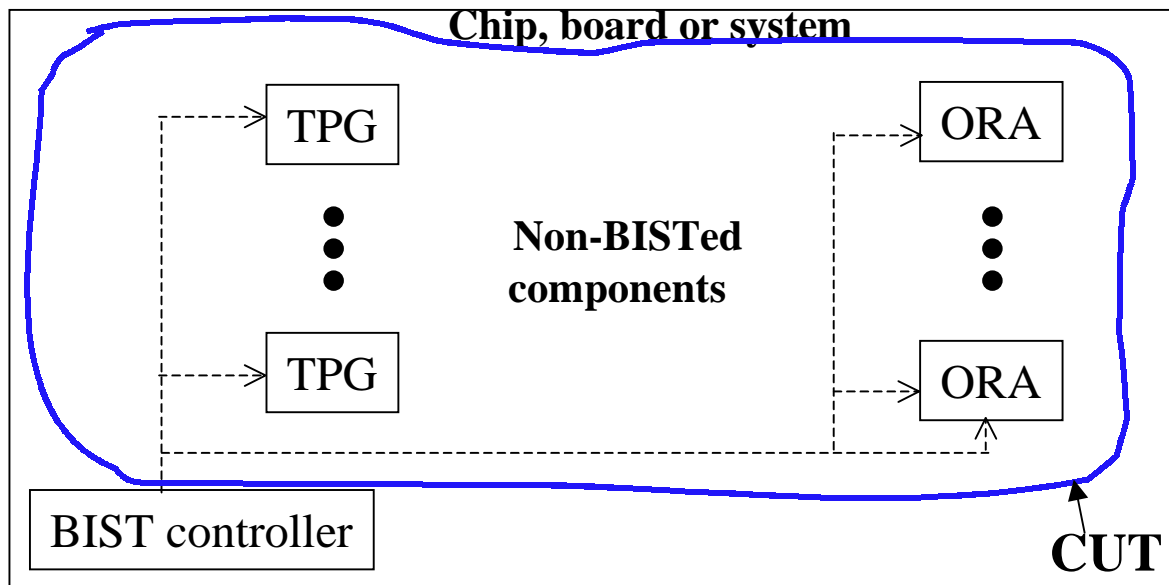- TPG and ORA are configured from among functional elements in the CUT
 - complex BIST controller
 - less hardware than distributed and separate architectures



Centralized and Embedded Architecture

- Test for attentiveness !
- Draw "centralized and embedded architecture" and show CUT



BIST Controller

- Single step CUT through some test sequences
- **Inhibit system** clocks and **control test** clocks
- Communicate with other test controllers using test buses
- Control self test operations
 - seeding of registers.
 - Keep track of the number of shift commands required in a scan operation
 - keep track of the number of test patterns processed




Choosing BIST Architecture

- Hints
 - low test time & degree of test parallelism--> distributed BIST
 - high FC -->distributed, customized TPG/ORAs to each CUT
 - level of packaging --> at higher levels use centralized BIST
 - physical constraints (size, weight, power, cooling) --> embedded & separate BIST requires more hardware, high performance degradation
 - complexity of replaceable units --> self testable replaceable units must contain TPG & ORAs.
 - If a system is the lowest level of replaceable units, then its constituent boards need not have TPG/ORAs and more centralized BIST arch. Can be used.
 - Factory and field test-and-repair strategy --> BIST affects type and usage of ATE
 - performance degradation --> BIST hardware in critical paths reduces the system clock rate



 Linear Feedback Shift Register (LFSR) - Example



S0	0	1	1
S1	0	0	1
S2	1	0	0
S3	0	1	0
S4	1	0	1
S5	1	1	0
S6	1	1	1
S7	0	1	1



Problems of Testing SoC

- Heterogeneous components - processors, memories, random logic.
- Core based design - reduced accessibility of internal structures
- increasing complexity - large amount of test data
- number of access ports - remains the same
- high speed/frequency - high demand on tester's driver/sensor mechanism
- deep submicron technology - complicated failure mechanism

- Solution --> BIST



Main Issues to be Considered in BIST for SoC

- Exploit existing circuits for BIST purpose to reduce hardware overhead
- optimize the BIST design with the rest of the circuit to avoid performance degradation
- share the same BIST components for different modules
- testing the BIST logic itself



The end

– ”BIST & DFT is fun and fine”

